



Computer Organization

Lab11 CPU Design(3)


‘single’ cycle CPU
clock, I/O



Topic


➤ CPU Design(3)

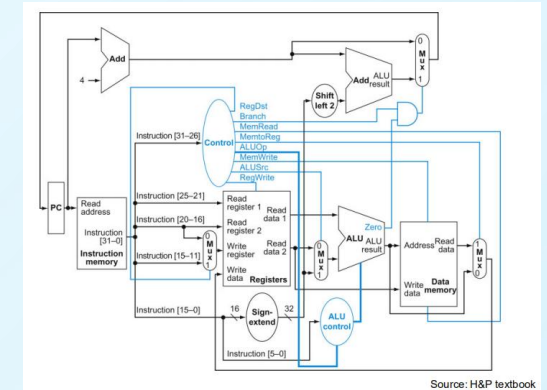- A 'single' cycle CPU 不是单周期，类似pipeline
- Clock (IP core)




➤ CPU work with I/O device

 - Option1: MMIO(Memory-Mapped IO)
 - MemOrIO, Controller +
- Option2: Specific Instruction
- Collaborative work between CPU and I/O



A 'single' cycle CPU

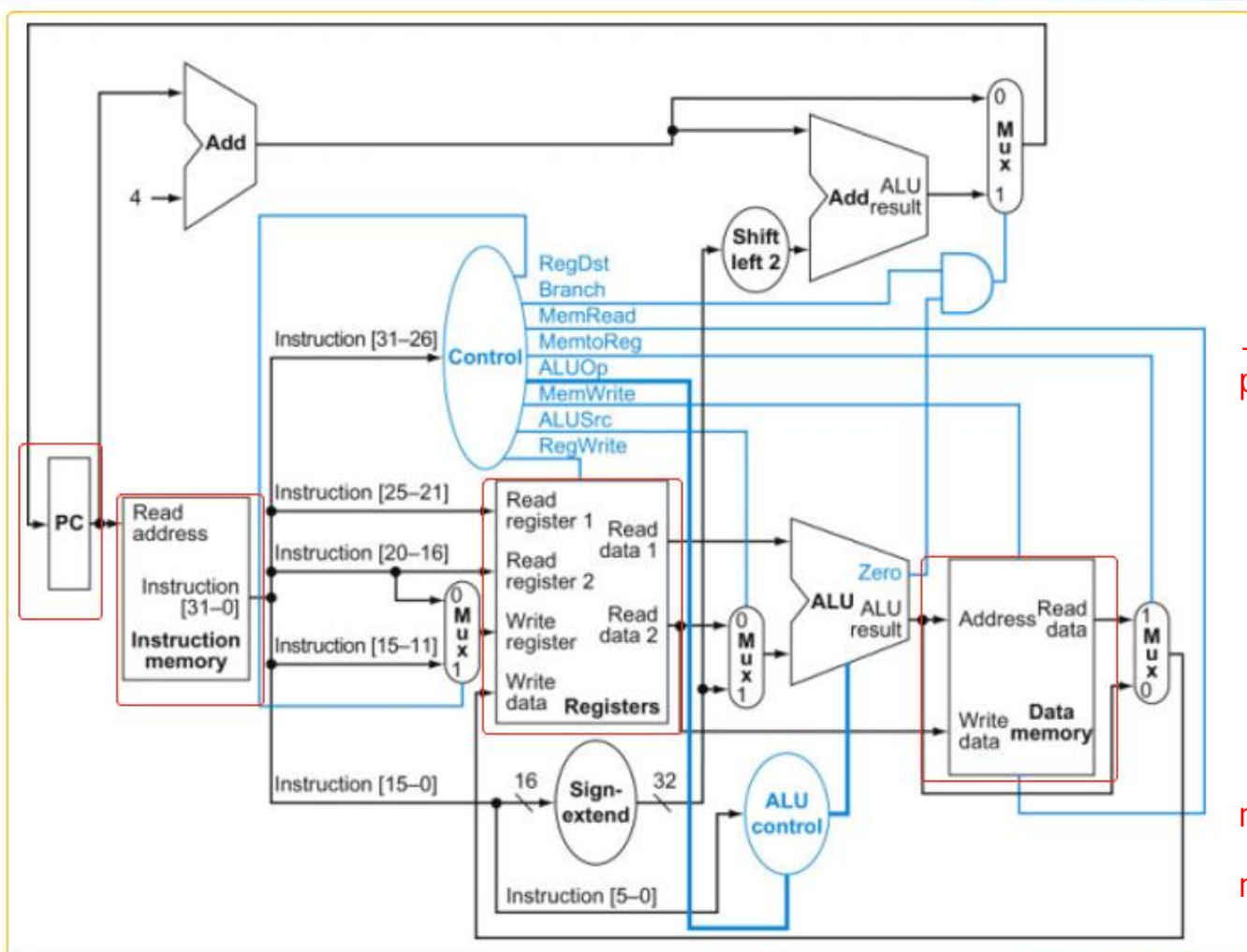

Source: H&P textbook

Q1. Does it **take time** for signals to be processed and transmitted within the module, as well as between modules?

Q2. Which sub modules within CPU **need the trigger from the clock**? When does the following event occur in a clock cycle?

- 1: neg
pos 1-1) **IFetch: update** the value of PC register
- 1-2) **IFetch: fetch** the instruction according to the value of PC
- 2-1-1) **Controller: generate the control signals**
- 2-2-1) **Decoder: get** the value of register(s)
- 2-2-2) **Decoder: generate** the extended immediate
- 3-1) **ALU: get** the operands
- 3-2) **ALU: generate** the calculaton result
- 4-1) **Dmemory: get** the **address**(from ALU) and **data**(from Decoder)
- 4-2) **Dmemory: read out** the data
- 5-1) **Decoder: write back** the data




Clock

➤ Add **PPL clock IP core** to generate the needed clock:

1. The clock on the Minisys/EGO1 development board is **100Mhz** *(clk_in1)*
➤ 100Mhz is too fast for a 'single' clock CPU

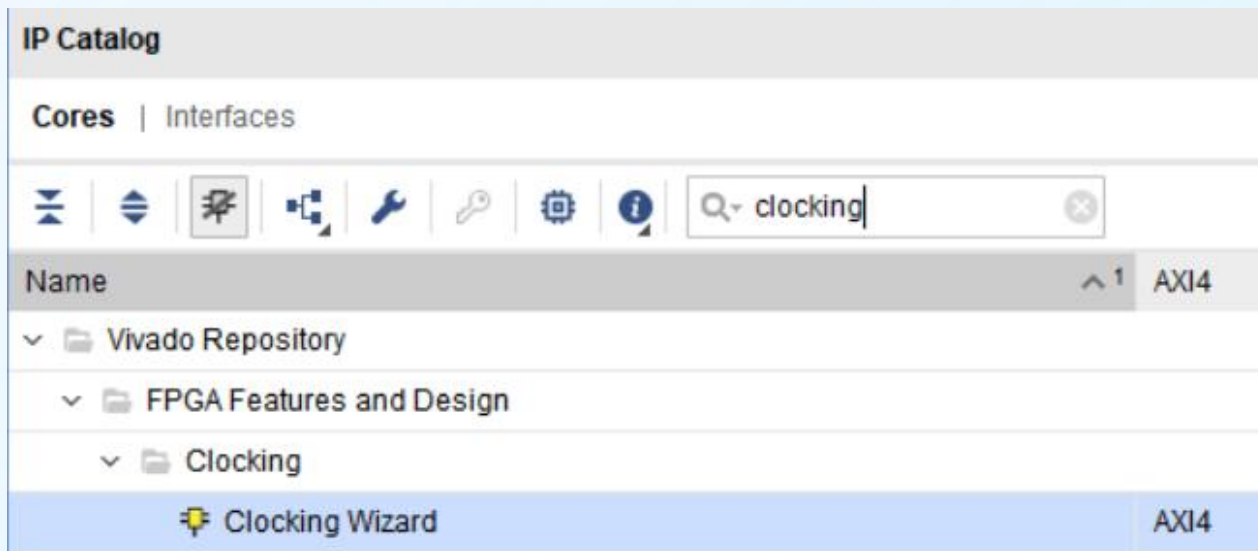2. A clock of 23Mhz is more suitable for the 'single' clock CPU *(clk_out1)*





Clock continued

Custom the IP core, set its **name**, **Primitive**, **Output Freq** and **with out the reset and locked**. Then **generate** the IP core with the settings.

Component Name **cpuck**

Clocking Options | Output Clocks | Port Renaming | PLL2 Settings | Summary

Clock Monitor

☐ Enable Clock Monitoring

Primitive

☐ MMCM ☒ **PLL**

Clocking Features

☒ Frequency Synthesis ☐ Minimize Power

☒ Phase Alignment

☐ Dynamic Reconfig

☐ Safe Clock Startup

Jitter Optimization

☒ Balanced

☐ Minimize Output Jitter

☐ Maximize Input Jitter filtering

Clocking Options | **Output Clocks** | Port Renaming | PLL2 Settings

The phase is calculated relative to the active input clock.

Output Clock	Port Name	Output Freq (MHz)	
		Requested	Actual
<input checked="" type="checkbox"/> clk_out1	clk_out1	23.000	23.000

Component Name **cpuck**

Clocking Options | **Output Clocks** | Port Renaming | PLL2 Settings | Summary

Enable Optional Inputs / Outputs for MMCM/PLL

☐ **reset** ☐ power_down

☐ **locked**

Reset Type

☒ Active High ☐ Active Low



The Function Verification of “cpuck”

Functional Verification by **testbench** and **simulator**

1) Create a verilog **testbench** module to instance the IP core “**cpuck**” and bind its ports. set the frequency of the input on “cpuck” as **100Mhz**.


2) Do the simulation to verify whether the output signal is a **23Mhz** clock signal while the input signal is **100Mhz**.

```
module cpuck_tb( ); // a reference testbench for 'cpuck'


    reg clk_in;
    wire clk_out;
    cpuck clk1( .clk_in1(clk_in), .clk_out1(clk_out) );

    initial      clk_in = 1'b0;
    always #5 clk_in=~clk_in;
endmodule
```

 NOTE: The output of IP core 'cpuck' need to work for a 'long' time to achieve stability.



Build and test the CPU

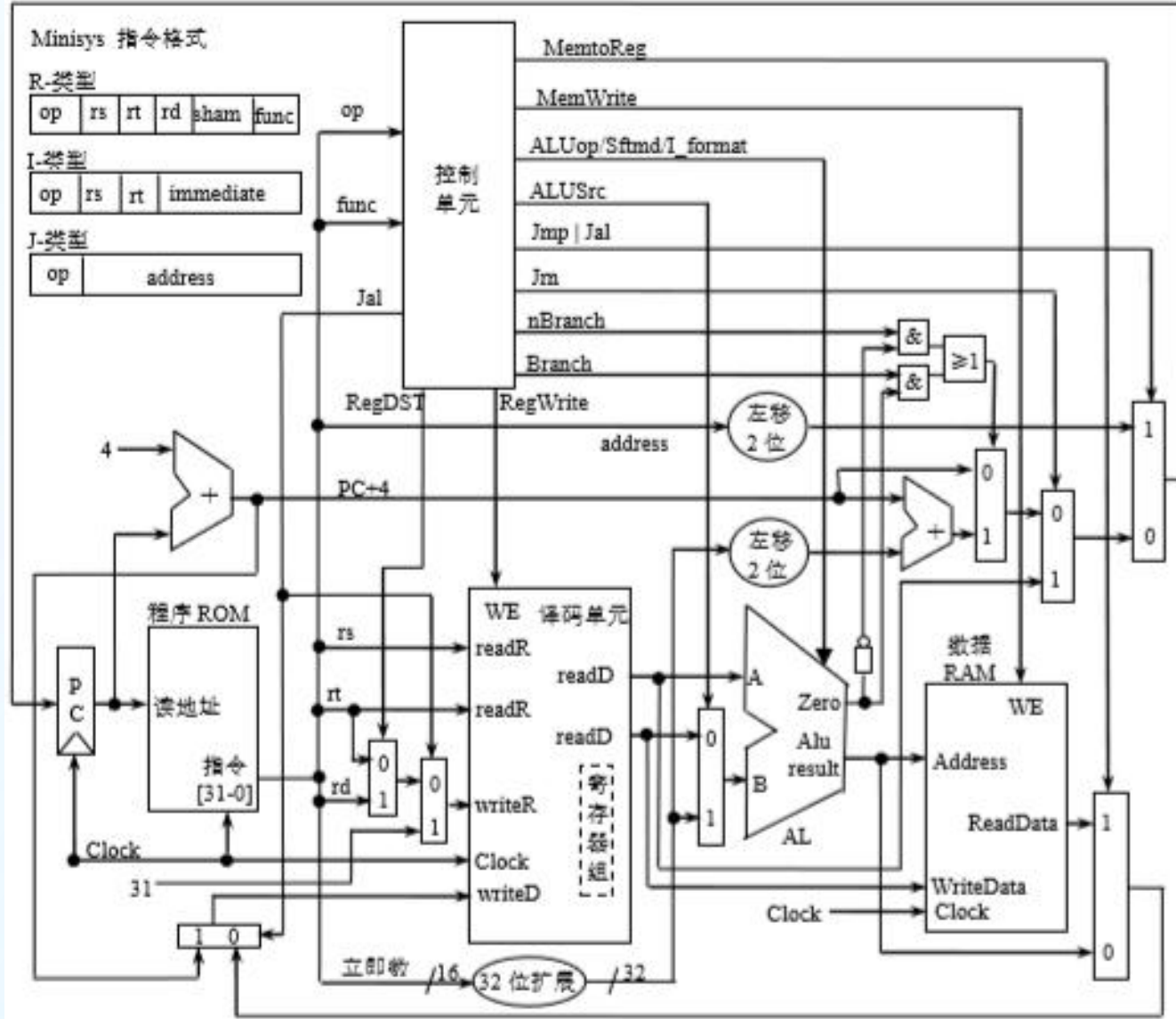

Build a CPU top module

1) **Instantiating** the sub-modules: **clock**, **Decoder**, execution unit/**ALU**, **IFetch**, **Controller** and **Data-Memory**.


2) Complete the inter-module connection inside the CPU and the **binding** to the CPU **port**.

Q1. How to test the CPU ?
how to determine the
program, the data, how to
check the testing result?




I/O interface

Minisys board with FPGA chip embedded

 


EGO1 board with FPGA chip embedded

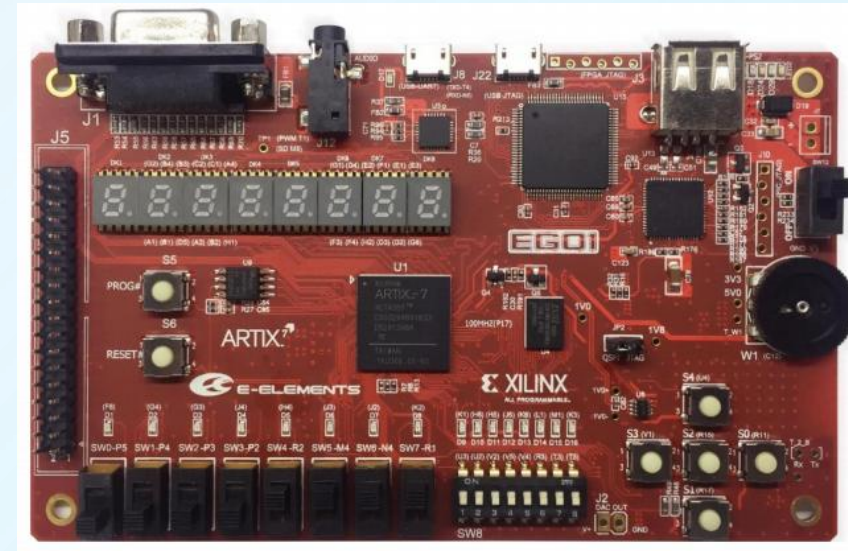

We have practiced a Cropped CPU on EGO1 in lab1

TIPS:

 
The handbook of board **Minisys** and **EGO1** could be found in the directory "labs\Handbook_of_Minisys_EGO1" on the course **BlackBoard** sit





CPU work with I/O

 - **Option1: MMIO**
 - lw/sw + $(2^{32} - 64K)$
 - MemOrIO
 - Controller + new control signals
- **Option2: Specific Instruction(s)**
 - Specific instruction(s)
 - $2^{(6+6)}$ - number of R,I,J type
 - e.g. syscall
- **Collaborative work between CPU and I/O**



Code	Basic	Source
0x24020008	addiu \$2,\$0,0x00000008	7: li \$v0,8 #to get a string
0x3c011001	lui \$1,0x00001001	8: la \$a0,sid
0x34240008	ori \$4,\$1,0x00000008	
0x24050009	addiu \$5,\$0,0x00000009	9: li \$a1,9
0x0000000c	syscall	10: syscall
0x24020004	addiu \$2,\$0,0x00000004	14: li \$v0,4 #to print a string
0x3c011001	lui \$1,0x00001001	15: la \$a0,s1
0x34240000	ori \$4,\$1,0x00000000	
0x0000000c	syscall	16: syscall
0x00000000	nop	18: nop
0x2402000a	addiu \$2,\$0,0x0000000a	20: li \$v0,10 #to exit
0x0000000c	syscall	21: syscall




A Simple Design on the I/O Interface

This part mainly accomplishes the following work:

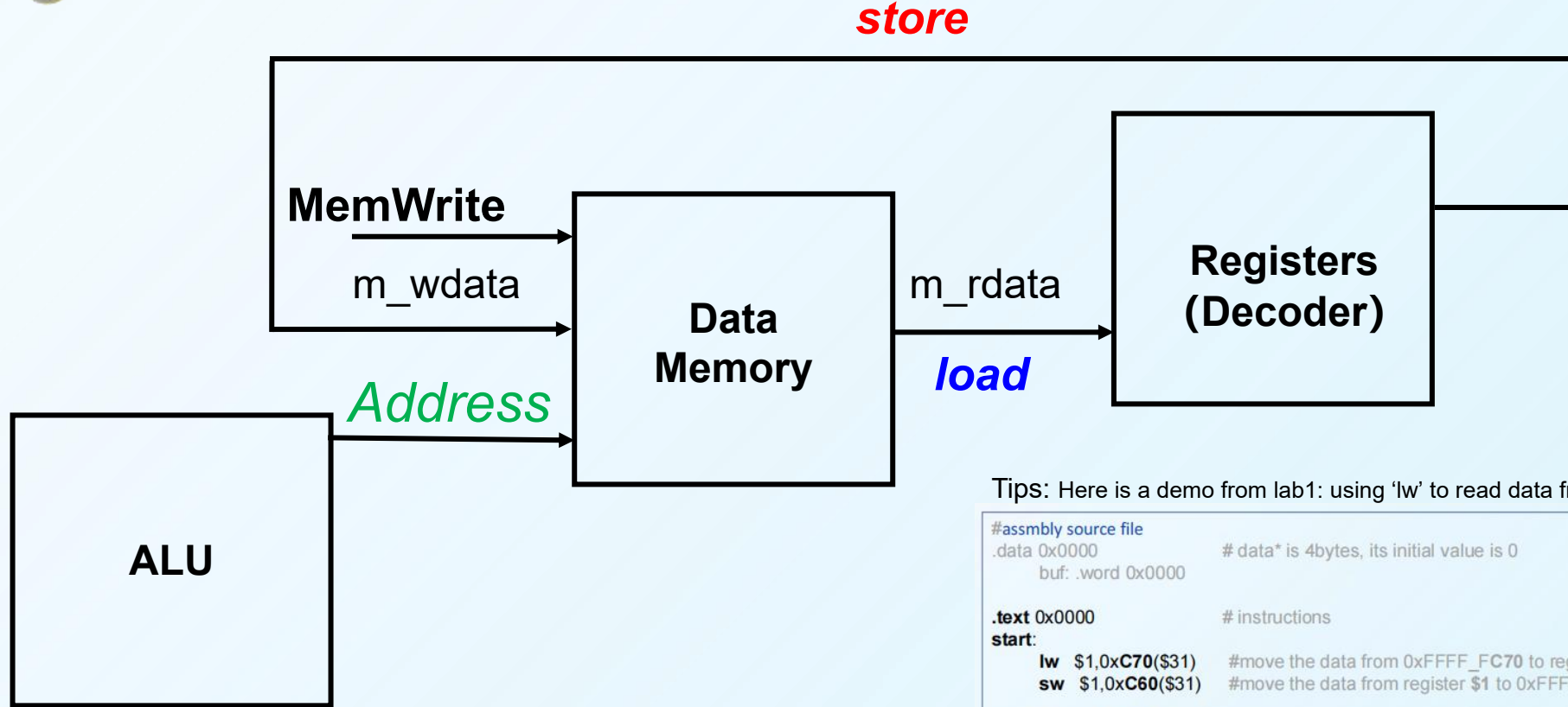1. Add I/O function
2. 16-bit LED design
3. 16-bit DIP Switch design

This is only one of the design solutions for I/O related data bus. Please develop a solution that suits your design needs

Option1: MMIO, reuse LW/SW to support I/O




Tips: Here is a demo from lab1: using 'lw' to read data from switches, 'sw' to write data to leds

```
#assembly source file
.data 0x0000          # data* is 4bytes, its initial value is 0
    buf: .word 0x0000

.text 0x0000          # instructions
start:
    lw $1,0xC70($31)   #move the data from 0xFFFF_FC70 to register $1
    sw $1,0xC60($31)   #move the data from register $1 to 0xFFFF_FC60


    lw $1,0xC72($31)
    sw $1,0xC62($31)

     j start            # jump to the instructions labled by start
```



NOTE:

 
- 1) There is no specific instruction in Minisys to read data from input ports and write data to output ports.
- 2) To implement the read/write process on I/O, it needs to **share the load/store instructions** in Minisys.



MMIO: I/O Share Part of the Data Bus Address

The space of **32** bits address bus is **4GB**(0x0000_0000~0xFFFF_FFFF)

 1024 bytes(0xFFFF_FC00~0xFFFF_FFFF) is designed to be allocated for the **I/O**.
Chip **Select** and **address** are specified by specifying **10** IO port lines.



Here is an example for **24 LED lights** and **24 DIP switches** on Minisys board, both of them are divided into two groups, all the ports in one group share the same address.

1. The CS(Chip Select) signal of the LED light is **ledCtrl**
2. The CS(Chip Select) signal of the DIP switch is **switchCtrl**

Range	LED(1~16)	LED(17~24)	Switch(1~16)	Switch(17~24)
Address	0xFFFFFC60	0xFFFFFC62	0xFFFFFC70	0xFFFFFC72



Note:

1. In the computer field, there are usually two schemes for I/O address space design: I/O and memory **unified addressing** or **I/O independent addressing**. However there is no dedicated I/ O instruction in current Minisys-1. Here, both LW and SW instructions are used for RAM access and I/O access, which means Minisys-1 can only use I/O unified addressing.

2. It is just a way for IO address implementation (MMIO: Memory-Mapped Input Output) , but not the only choice.



CPU: add a new module - MemOrIO

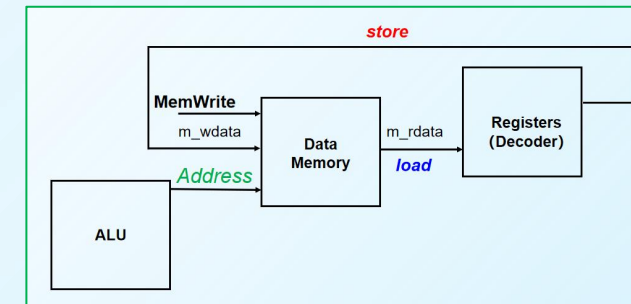 


MemOrIO determine:

- 1). The destination of **r_rdata**
- 2). The source of **r_wdata**

Chip Select signal
LedCtrl (0xFFFFFC60, 0xFFFFFC62)
SwitchCtrl (0xFFFFFC70, 0xFFFFFC72)...



MemOrIO continued

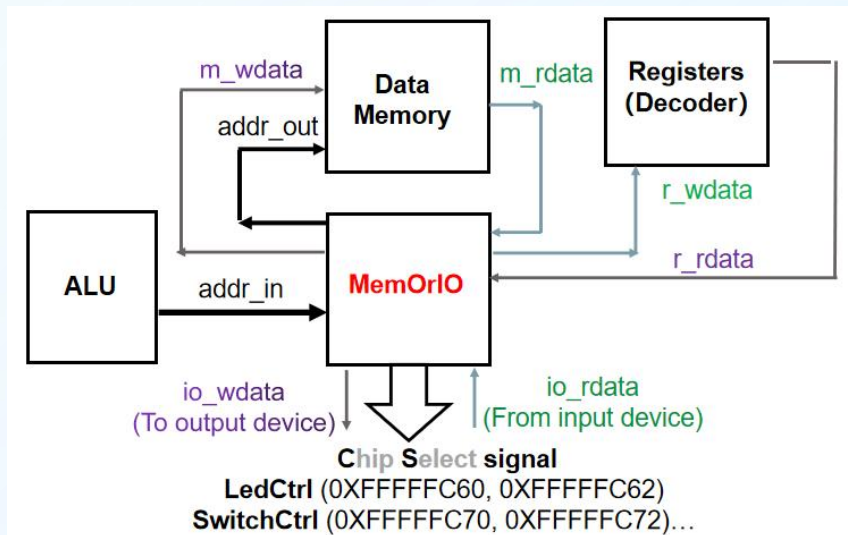

```
module MemOrIO( mRead, mWrite, ioRead, ioWrite, addr_in, addr_out,
m_rdata, io_rdata, r_wdata, r_rdata, write_data, LEDCtrl, SwitchCtrl);

input mRead;           // read memory, from Controller
input mWrite;          // write memory, from Controller
input ioRead;          // read IO, from Controller
input ioWrite;         // write IO, from Controller

input[31:0] addr_in;   // from alu_result in ALU
output[31:0] addr_out; // address to Data-Memory


input[31:0] m_rdata;   // data read from Data-Memory
input[15:0] io_rdata;  // data read from IO, 16 bits
output[31:0] r_wdata;  // data to Decoder(register file)

input[31:0] r_rdata;   // data read from Decoder(register file)
output reg[31:0] write_data; // data to memory or I/O (m_wdata, io_wdata)
output LEDCtrl;       // LED Chip Select
output SwitchCtrl;    // Switch Chip Select
```

*Tips: A demo about how the **Chip Select** signals work on I/O could be found in **labs/lab11_io** on course BlackBoard site*



MemOrIO continued

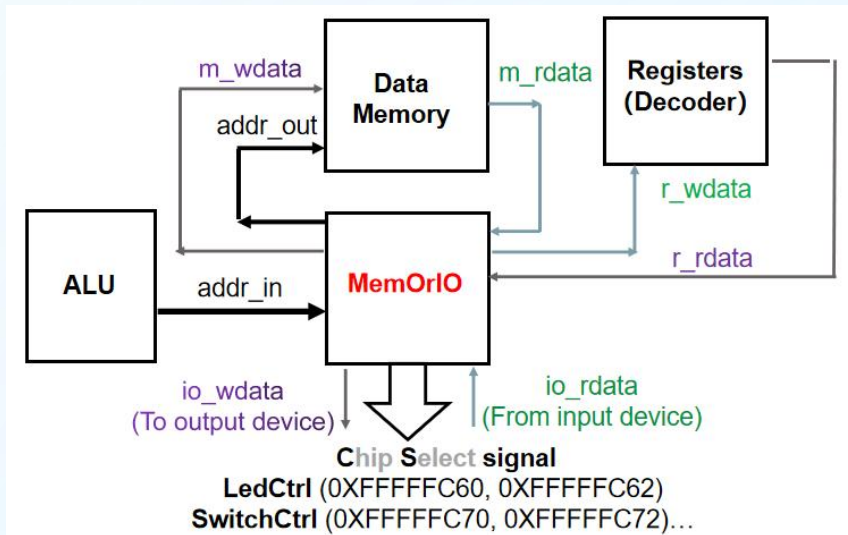

```
assign addr_out= addr_in;  
// The data write to register file may be from memory or io.  
// While the data is from io, it should be the lower 16bit of r_wdata.  
assign r_wdata = ? ? ?
```


```
// Chip select signal of Led and Switch are all active high;  
assign LEDCtrl= ? ? ?  
assign SwitchCtrl= ? ? ?
```

```
always @* begin  
    if((mWrite==1)||(ioWrite==1))  
        //write_data could go to either memory or IO. where is it from?  
        write_data = ? ? ?  
    else  
        write_data = 32'hZZZZZZZZ;  
end  
endmodule
```

The Function Verification of MemOrIO

```
// a reference for the testbench of MemOrIO
module MemOrIO_tb( );
    reg mRead,mWrite,ioRead,ioWrite;
    reg[31:0] addr_in,m_rdata,r_rdata;
    reg[15:0] io_rdata;
    wire LEDCtrl,SwitchCtrl;
    wire [31:0] addr_out,r_wdata,write_data;
```
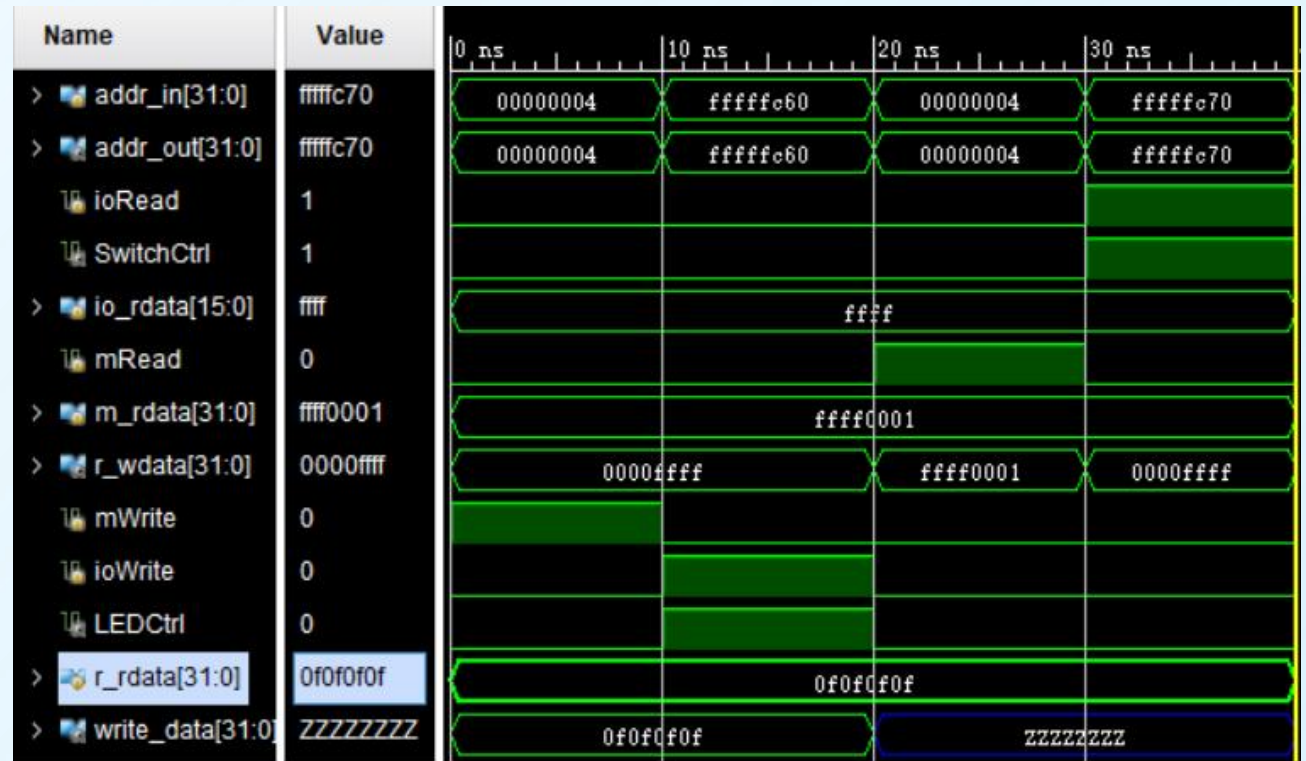
```
    MemoryOrIO umio(addr_out, addr_in,
mRead, mWrite, ioRead, ioWrite,
m_rdata, io_rdata, r_rdata, r_wdata, write_data,
LEDCtrl, SwitchCtrl );
```




```
initial begin // r_rdata -> m_wdata(write_data)
    m_rdata = 32'h0xffff_0001; io_rdata = 16'h0xffff; r_rdata = 32'h0x0f0f_0f0f; addr_in = 32'h4; {mRead,mWrite,ioRead,ioWrite}= 4'b01_00;
    #10 addr_in = 32'hffff_fc60; {mRead,mWrite,ioRead,ioWrite}= 4'b00_01; // r_rdata -> io_wdata(write_data)
    #10 addr_in = 32'h0000_0004; {mRead,mWrite,ioRead,ioWrite}= 4'b10_00; // m_rdata -> r_wdata
    #10 addr_in = 32'hffff_fc70; {mRead,mWrite,ioRead,ioWrite}= 4'b00_10; // io_rdata -> r_wdata(write_data)
    #10 $finish;
end
endmodule
```




Controller+

 Add new ports to Controller for IO reading and writing support.



```
module control32(Opcode,Function_opcode,Jr,Branch,nBranch,Jmp,Jal,
Alu_resultHigh,
RegDST, MemorIOtoReg, RegWrite,
MemRead, MemWrite,
IORead, IOWrite,
ALUSrc,ALUOp,Sftmd,I_format);
...
input[21:0] Alu_resultHigh; // From the execution unit Alu_Result[31..10]
output MemorIOtoReg; // 1 indicates that data needs to be read from memory or I/O to the register
output RegWrite; // 1 indicates that the instruction needs to write to the register
output MemRead; // 1 indicates that the instruction needs to read from the memory
output MemWrite; // 1 indicates that the instruction needs to write to the memory
output IORead; // 1 indicates I/O read
output IOWrite; // 1 indicates I/O write
...
```



Controller+ continued

- 1) **Modify** the logic of the '**MemWrite**'
- 2) **Add** '**MemRead**', '**IORead**' and '**IOWrite**' signals
- 3) **Change** '**MemtoReg**' to '**MemorIotoReg**'.

```
// The real address of LW and SW is Alu_Result, the signal comes from the execution unit
// From the execution unit Alu_Result[31..10], used to help determine whether to process Mem or IO
input[21:0] Alu_resultHigh;

output    MemorIotoReg;    //1 indicates that read data from memory or I/O to write to the register
output    MemRead;        // 1 indicates that reading from the memory to get data
output    IORead;         // 1 indicates I/O read
output    IOWrite;        // 1 indicates I/O write

assign RegWrite = (R_format || Lw || Jal || I_format) && !(Jr) ;    // Write memory or write IO
assign MemWrite = ((sw==1) && (Alu_resultHigh[21:0] != 22'h3FFFFFF)) ? 1'b1:1'b0;
assign MemRead = ? ? ?    // Read memory
assign IORead = ? ? ?    // Read input port
assign IOWrite = ? ? ?    // Write output port

// Read operations require reading data from memory or I/O to write to the register
assign MemorIotoReg = IORead || MemRead;
```



Option2: Specific instruction for I/O

- Use **specific instructions** and **independent address spaces** to access and address I/O devices(e.g. IN/OUT instructions used in x86 ISA to access the I/O device)
- Implementation the solution about Specific instruction for I/O on Minsys
 - **ISA** (add new instructions about I/O access)
 - **Assembler** (recognizes and supports the added instructions)
 - **CPU** (Modification)
 - **Control Path**
 - Controller: **distiguish the IO and the data-memory by the opcode and function code in the instruction instead of the address calculated by the ALU**
 - The **control signal** to the Data Path
 - **Data Path**
 - The **data path** between the **Decoder, Data-Memory, I/O module** and **ALU**

How about 'syscall' ??
(0x0000_000c)



Collaborative work between CPU and I/O

How to collaborate between IO devices and CPUs?


- Issue1: speed mismatch between sender and receiver
 - solution: cache, fifo
- Issue2: out of sync on the communication between sender and receiver

➤ solution1 of issue2

Polling between waiting and checking:

- **when the condition(s) is(are) met**(e.g. the input data is ready), **continue the regular process**
- **when the condition(s) is(are) NOT met**, **do nothing except checking while 'waiting'**.

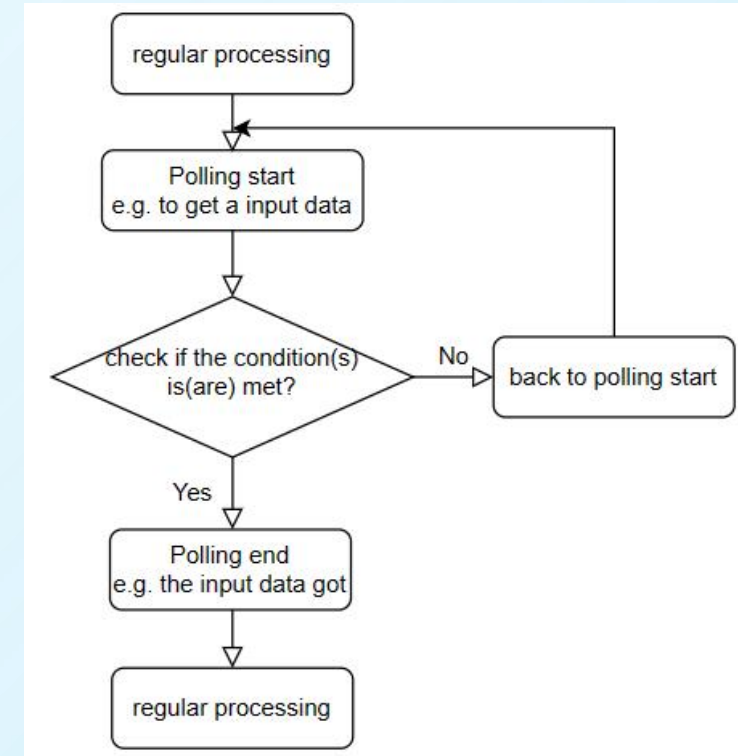
How to 'wait' ??
What's your solution about 'wait' ??



Collaborative work between CPU and I/O continued

Solution2 on the issue2(out of sync on the communication between sender and receiver)

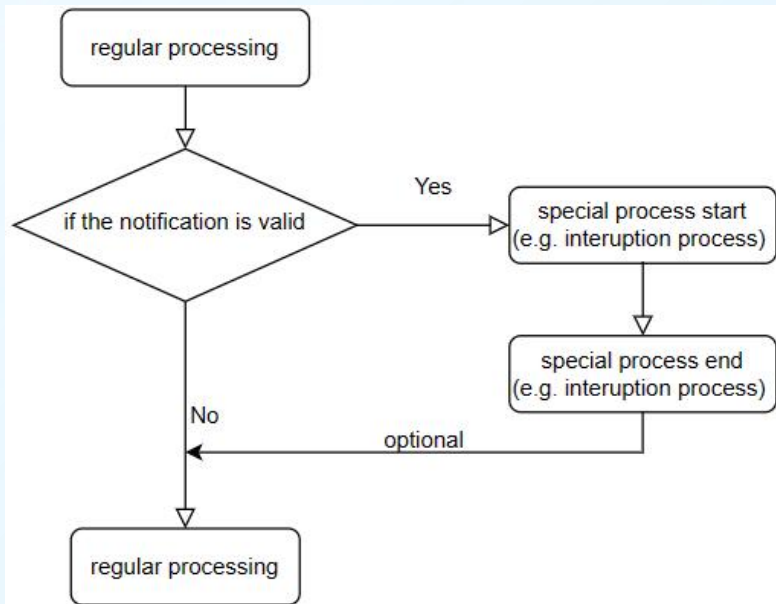- When there is **NO** notification, do regular process (other things) first.
- When there is a **notification**
 - **stop for specialtreatment**(e.g. excepton/interrupt process)
 - after finish the specialtreatmen then return to(optional) the regular process to continue.



- How to Generate and identify the notification(s)?
 - The internal signals of CPU
 - e.g. exception about overflow (generated by the ALU)
 - The external signals of CPU
 - e.g. interruption from input device

Which module(s) in CPU receive and identify the notification ? ?

- How to 'wait'?
 - do something but meaningless
 - nop (sll \$0,\$0,0) 32-bit 全0
 - do nothing
 - adding chipsel / enable control on the sub-modules in CPU

用if else

Which solution about wait lead to lower power consumption ??

- How to determine the waiting time?
 - The time of the instruction cycle * the number of instructions



Practice

P1-1. Do the functional verification on the module `cpuclk`(which is introduced on the first part of this lab)

P1-2. Answer the Q2 on page 2 and Q1 on page 7 of this lab slides.

P2. Complete the following modules, do the function verification:

- 1. MemoryOrIO
- 2. Controller+
- 3. Single cycle CPU with I/O process

P3. Redesign and implement the solution about I/O data bus and I/O addressing that are suitable for your design. Build the single cycle CPU with the updated solution of I/O process and do the function verification.

P4. Design the solution on collaborate between IO devices and CPU in your teamwork of CPU, evaluate work in software and hardware collaborative development.